

## Honors Physics Electric Circuits HW, part 2 (Homework)

For help with these problems

[www.tutor-homework.com](http://www.tutor-homework.com)

Be sure to mention the filename:

Physics\_Questions\_0067

[www.tutor-homework.com](http://www.tutor-homework.com) (for tutoring, homework help, or help with online classes)

1.

A  $9.90\text{-V}$  battery delivers  $106\text{ mA}$  when connected to a  $61.0\text{-}\Omega$  load. Determine the internal resistance of the battery.

2.

An  $15\text{ }\Omega$  resistor and a  $9.0\text{ }\Omega$  resistor are connected in series across an  $15\text{ V}$  battery.

(a) Find the current through each resistor and the voltage drop across each resistor.

Currents

Voltage Drops

(b) Repeat part (a) for the situation in which the resistors are connected in parallel across the  $15\text{ V}$  battery.

Currents

Voltage Drops

3.

A  $9.3\text{-}\Omega$  resistor and a  $5.6\text{-}\Omega$  resistor are connected in series with a power supply.

(a) The voltage drop across the  $5.6\text{-}\Omega$  resistor is measured to be  $10\text{ V}$ . Find the voltage output of the power supply.

(b) The two resistors are connected in parallel across a power supply, and the current through the  $9.3\text{-}\Omega$  resistor is found to be  $0.25\text{ A}$ . Find the voltage setting of the power supply.

4.

What is the equivalent resistance of the combination between points  $a$  and  $b$  in Figure P18.7? Note that one end of the vertical resistor is left free.

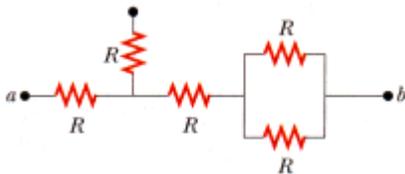


Figure P18.7.

5.

- (a) Find the equivalent resistance of the circuit in Figure P18.9.  
 (b) If the total power supplied to the circuit is  $3.00 \text{ W}$ , find the emf of the battery.

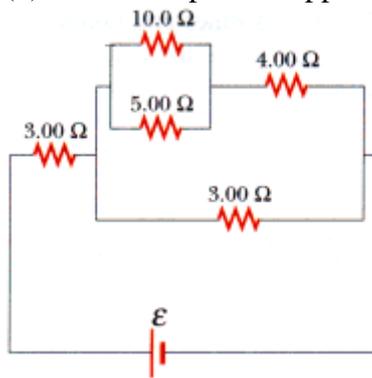


Figure P18.9.

6.

The resistance between terminals  $a$  and  $b$  in Figure P18.13 is  $85 \Omega$ . If the resistors labeled  $R$  have the same value, determine  $R$ .

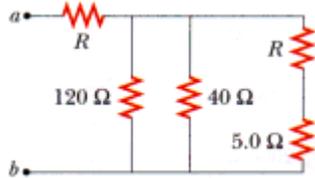


Figure P18.13

7.

Determine the potential difference,  $\Delta V_{ab}$ , for the circuit in Figure P18.15.

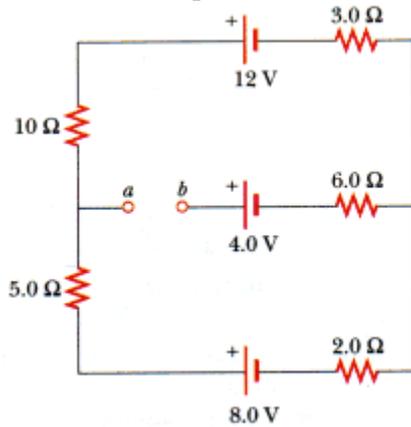


Figure P18.15.

8.

In the circuit of Figure P18.17, the current  $I_1$  is  $3 \text{ A}$  while the values of  $\mathcal{E}$  and  $R$  are unknown. What are the currents  $I_2$  and  $I_3$ ?

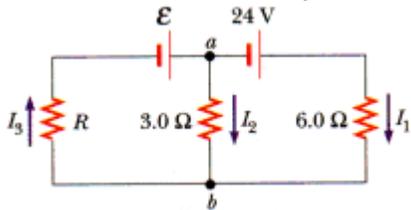


Figure P18.17.

9.

In the circuit shown in Figure P18.17, the current  $I_1$  is 3 A and  $R = 15 \Omega$ . What is the emf,  $\mathcal{E}$ , of the unknown battery?

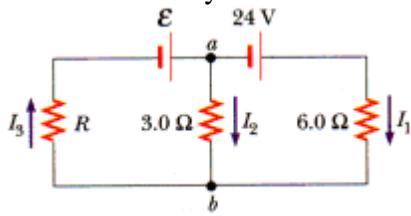


Figure P18.17

10.

Two 1.70-V batteries--with their positive terminals in the same direction--are inserted in series into the barrel of a flashlight. One battery has an internal resistance of  $0.290 \Omega$ , the other an internal resistance of  $0.159 \Omega$ . When the switch is closed, a current of 0.600 A passes through the lamp. (See the note in Problem 8.)

(a) What is the lamp's resistance?

(b) What fraction of the power dissipated is dissipated in the batteries?

11.

Calculate each of the unknown currents  $I_1$ ,  $I_2$ , and  $I_3$  for the circuit of Figure P18.23. (Figure next page.)

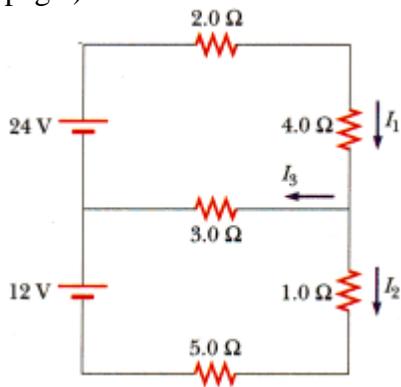


Figure P18.23.